


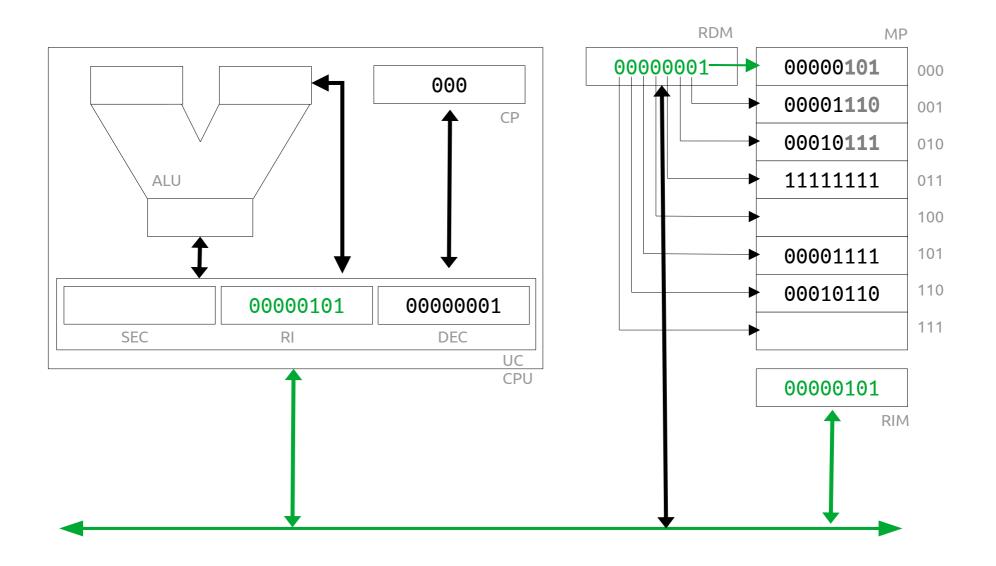



0	0	0	1	0	0	0	0	0	0	0
				1						
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
				0						
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

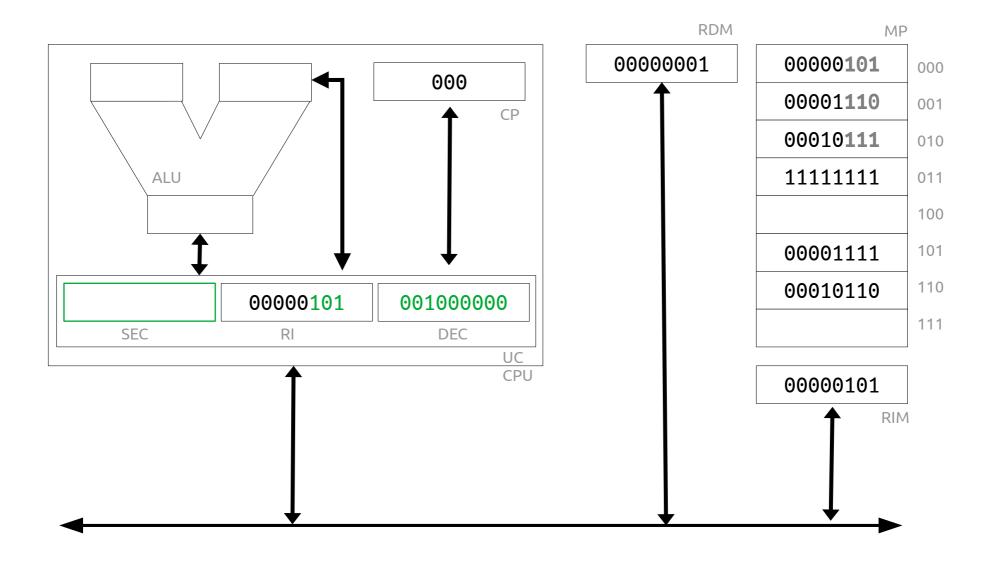


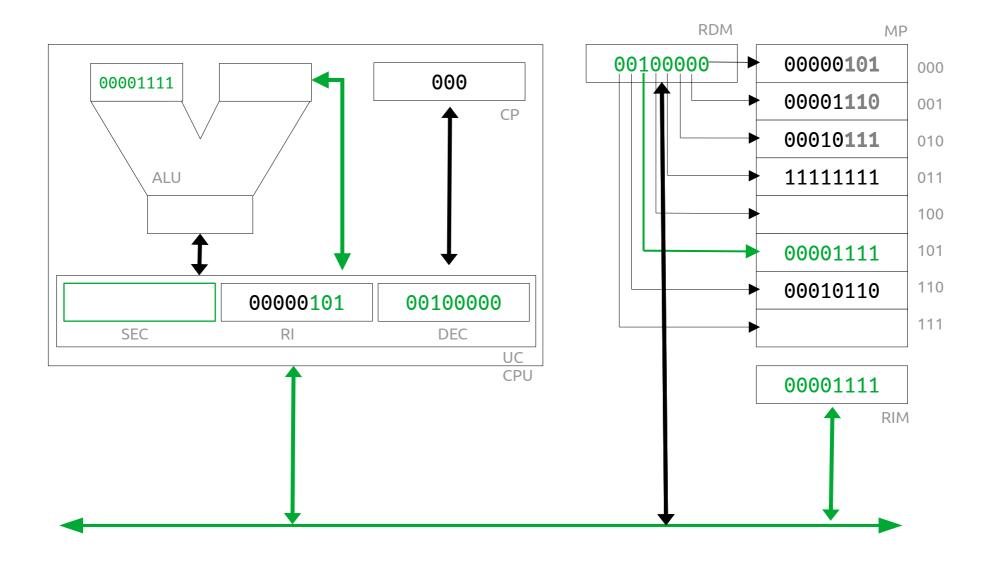

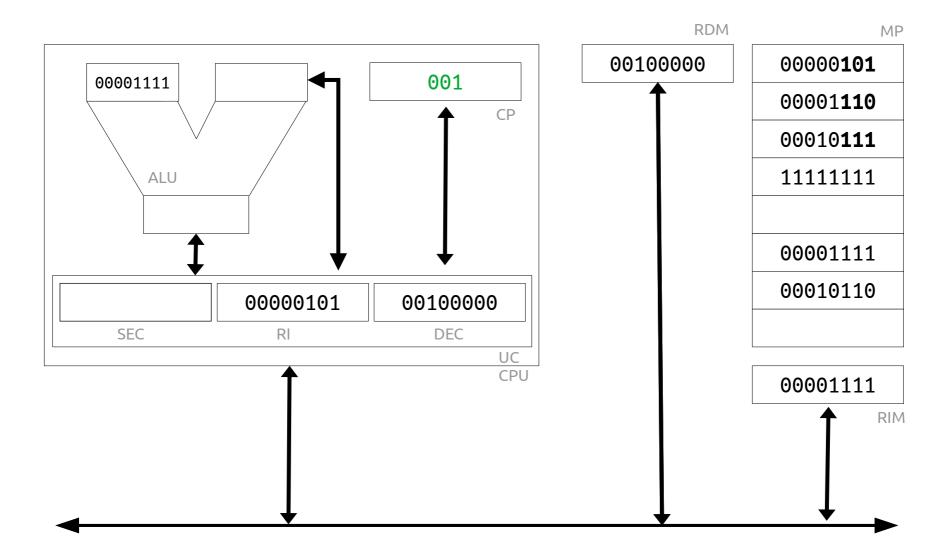



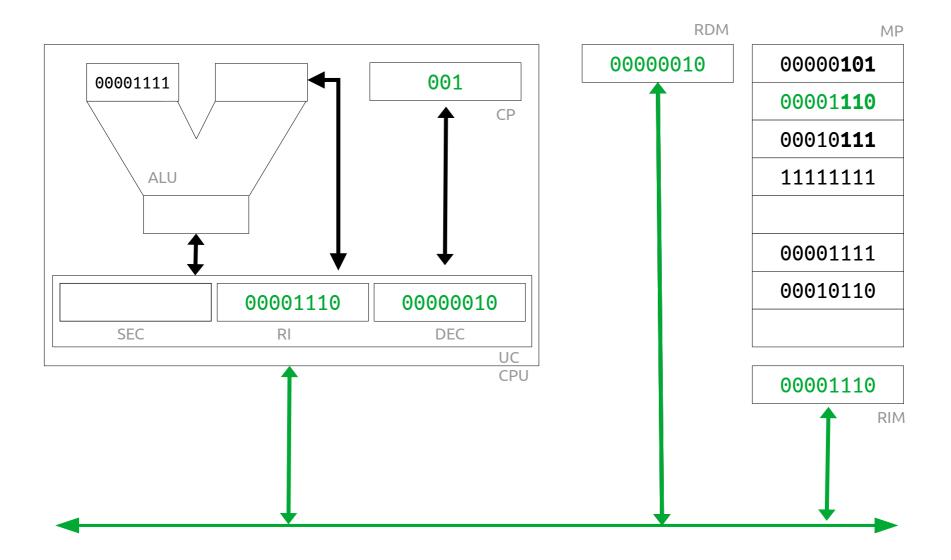


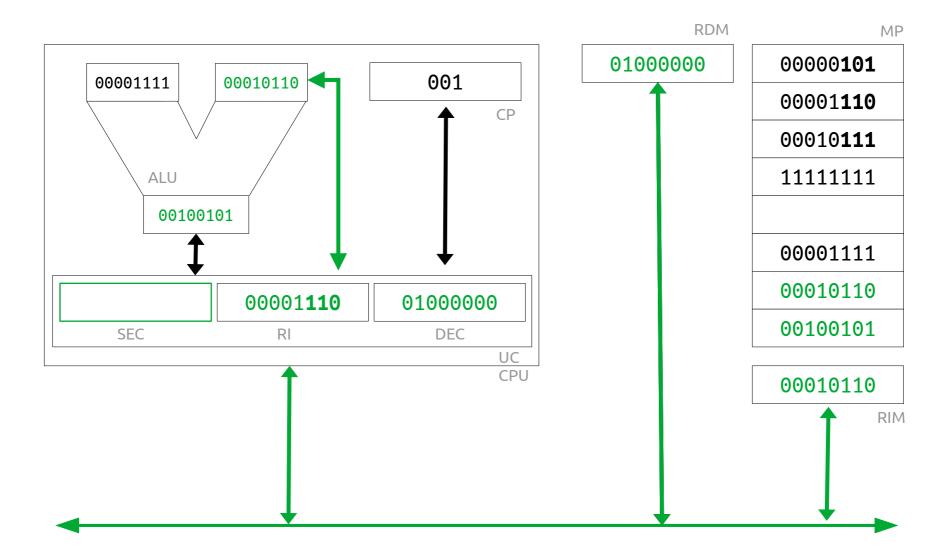



Sumador con acarreo

С	a	b	S	$C_{\scriptscriptstyle{+}}$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1
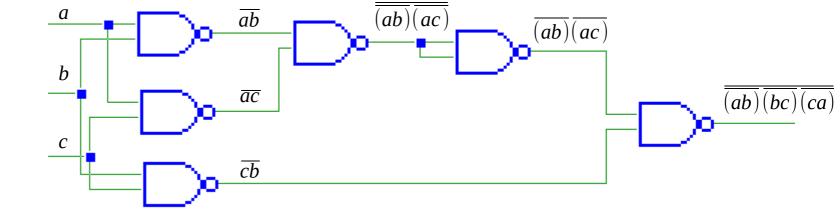
$$C_{+} = cb + ab + ca = (negamos \ dos \ veces) = \overline{cb + ab + ca} = (morgan) = \overline{(ab)(bc)(ca)}$$



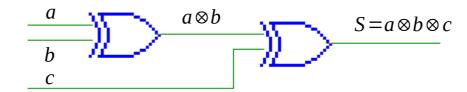


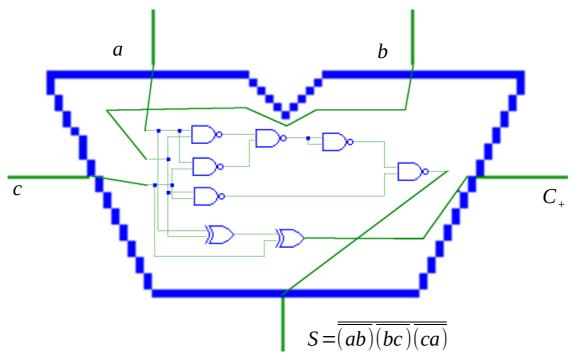



Suma de n bits:


$$a=(a_1,a_2,\ldots,a_n)$$


$$b=(b_1,b_2,\ldots,b_n)$$

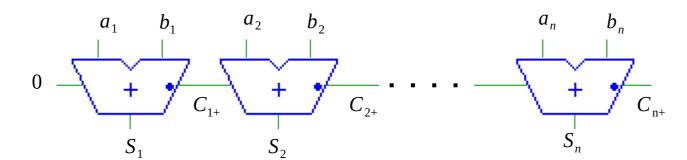


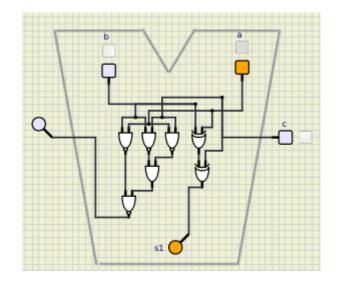


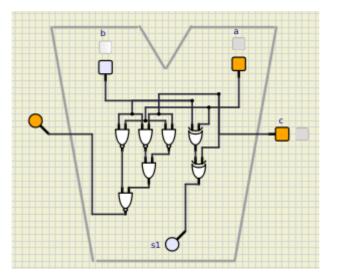


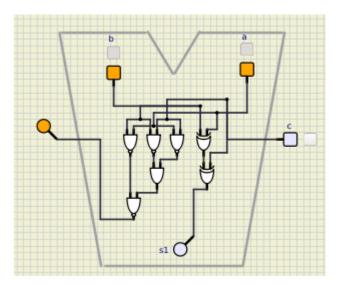


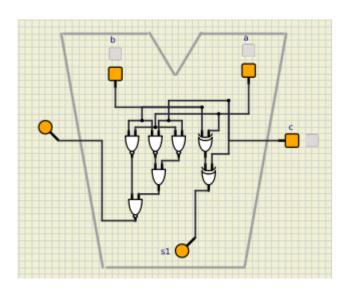

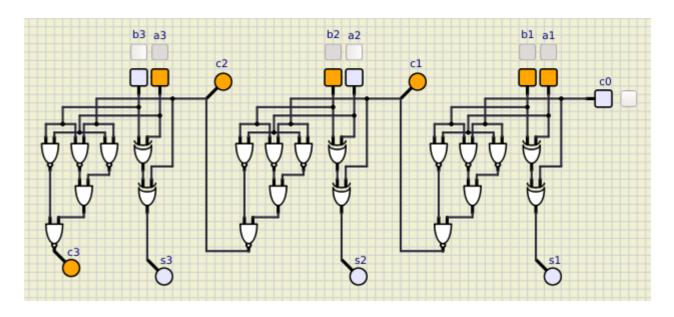


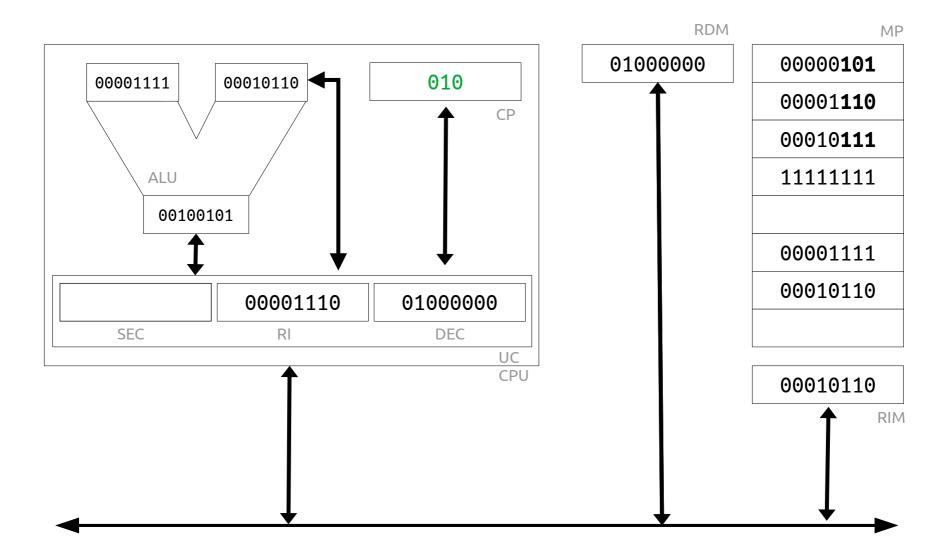


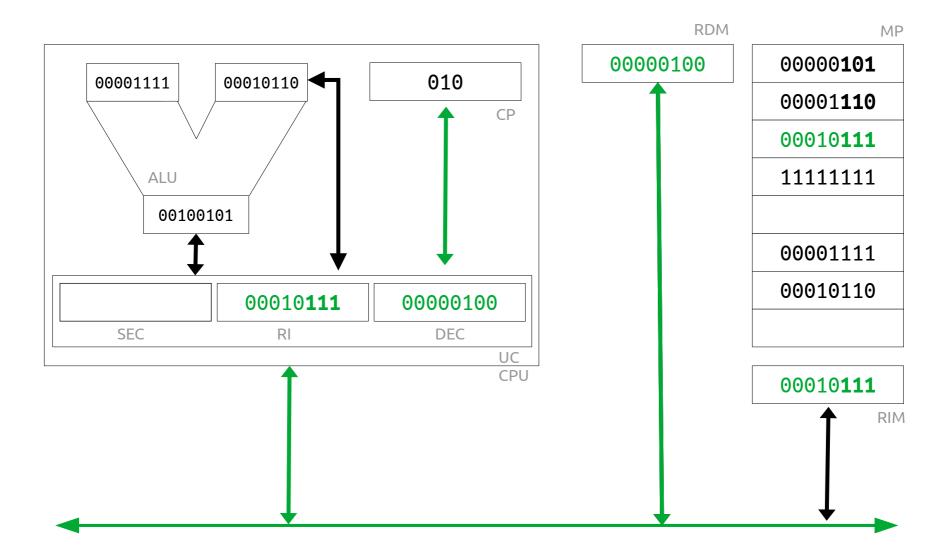


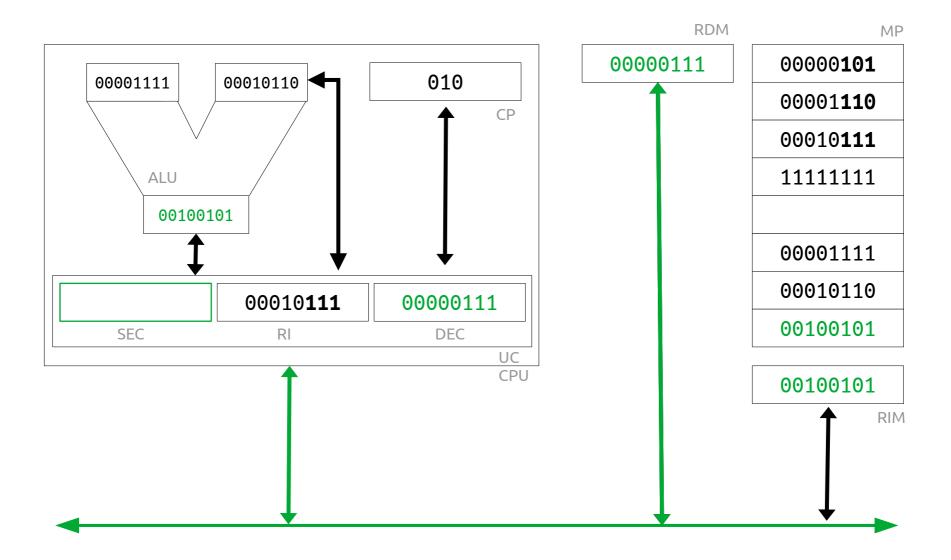



La memoria

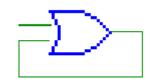


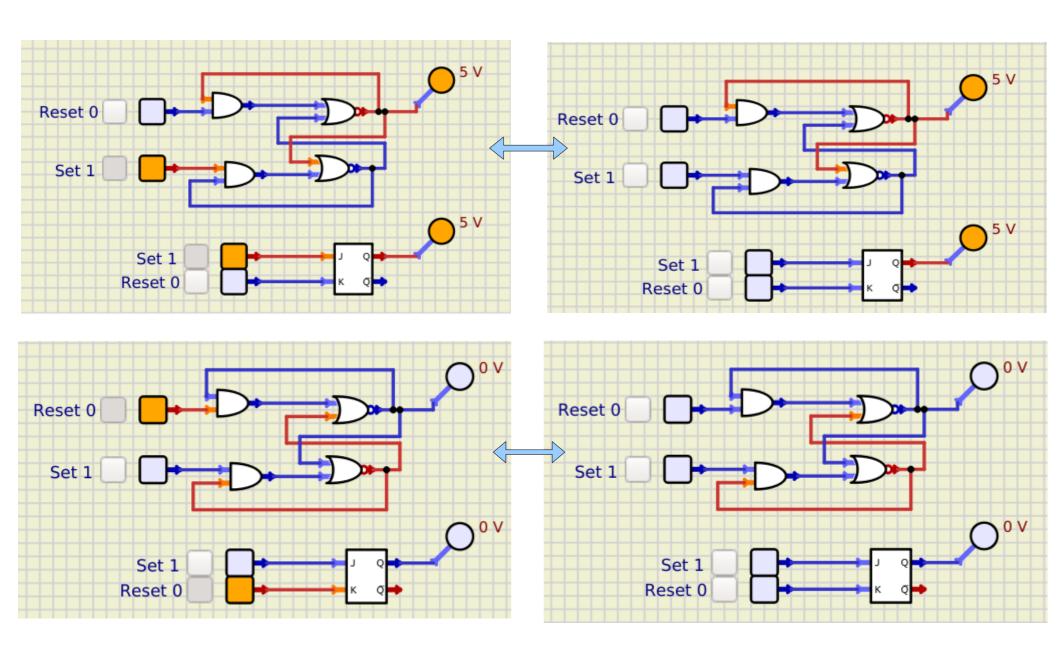

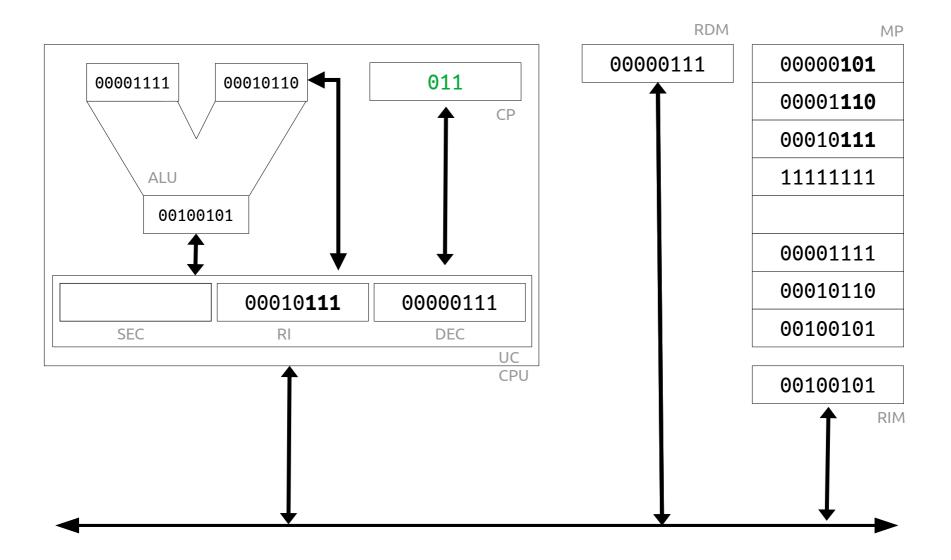

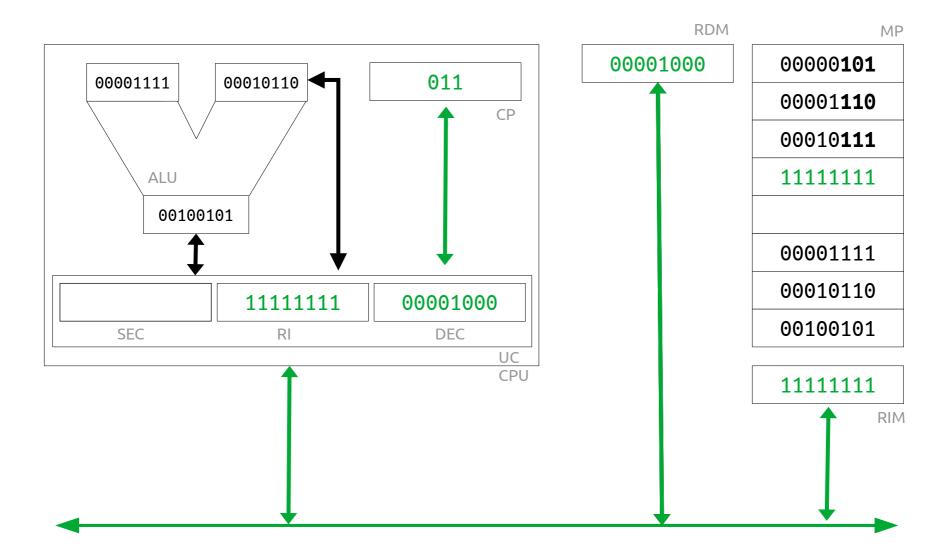

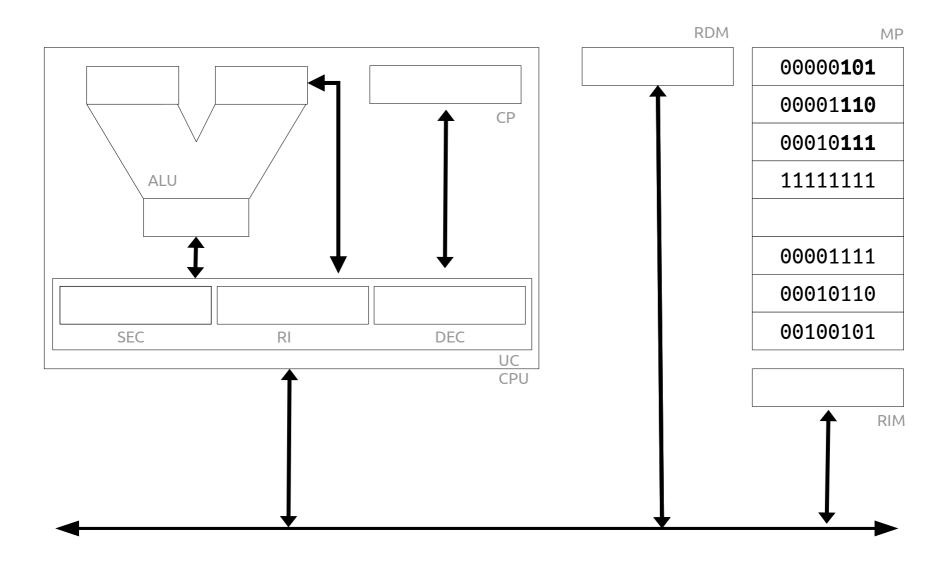

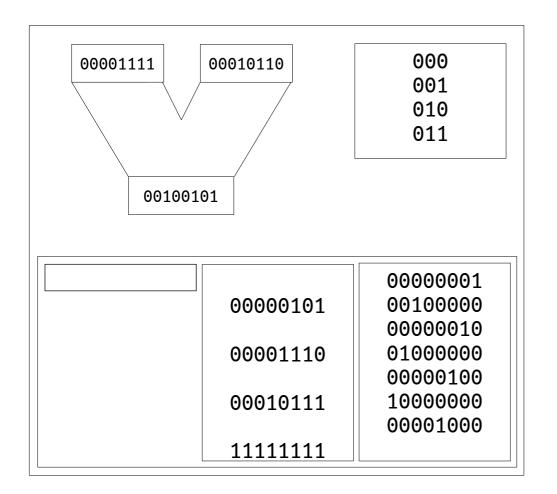

00000101
00001110
00010111
11111111
00001111
00010110
00100101

